

## **SUBJECT: BASIC ELECTRONICS ENGINEERING**

### **Part-I**

Q1 Answer the following questions: (2 x 10)

- a) Explain the depletion region in p-n diode.
- b) Differentiate between clipper and clamper circuit.
- c) Why the emitter region of a transistor is more heavily doped than the base region?
- d) "BJT is current controlled while FET is voltage controlled". Justify.
- e) Mention advantages and limitations of integrated circuits.
- f) Draw the equivalent circuit of ideal Op-Amp.
- g) What is CMRR in Op-Amp? Mention its value in ideal Op-Amp.
- h) Determine the hexadecimal equivalent of 26.25.
- i) State and prove De Morgan's theorem.
- j) Discuss Absorption theorem present in Boolean algebra.

### **Part-II**

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- a) Draw the equivalent circuit of Si p-n diode. Discuss the procedure to find the equivalent circuit.
- b) With neat circuit diagram, describe the operation of bridge rectifier. Calculate its PIV.
- c) Show the width and doping profile of a transistor. Justify your answer. Draw the symbol of p-n-p and n-p-n transistor.
- d) Discuss how a transistor can be used as a voltage amplifier.
- e) For an n-channel D- and E-MOSFET
  - I. Draw the structure and corresponding symbol.
  - II. Draw Drain and transfer characteristics curve with proper voltage and current notations.
  - III. Mention output current expression.

- f) Explain the principle of operation of a digital inverter.
- g) I. If  $\beta = 16.5$ ,  $I_E = 1.8 \text{ mA}$  and  $I_{CO} = 12 \mu\text{A}$ , calculate  $I_C$  and  $I_B$  when the transistor is used in the CE configuration.
- II. For a p-n-p transistor in CE mode,  $\beta = 100$ . What is the value of  $\alpha$ ? If  $I_{CO} = 10 \mu\text{A}$ ,
- III. What is the collector current for an emitter current of 2 mA?
- h) Draw inverting configuration using Op-Amp. Calculate the voltage gain of the circuit for  $v_i = 150 \text{ mV rms}$ ,  $R_f = 75 \text{ K}\Omega$  and  $R_i = 36 \text{ K}\Omega$ . For the same parameter, calculate the voltage gain of non-inverting amplifier.
- i) Compute the output voltage of the circuit shown in figure-1 for  $V_{in1} = 0.2 \text{ V}$ ,  $V_{in2} = -0.5 \text{ V}$ ,  $V_{in3} = 0.8 \text{ V}$ ,  $R_1 = 33 \text{ K}\Omega$ ,  $R_2 = 22 \text{ K}\Omega$ ,  $R_3 = 12 \text{ K}\Omega$ , and  $R_4 = 68 \text{ K}\Omega$ . Figure-1
- j) I. Subtract  $(29)_{10}$  from  $(15)_{10}$  using 2's complement method of subtraction.
- II. Subtract  $(25)_{10}$  from  $(8)_{10}$  using 1's complement method of subtraction.
- k) Convert the following:
- I. (FACE)<sub>16</sub> = (?)<sub>10</sub>
- II.  $(65.45)_{10} = (?)_2$
- III.  $(1111011011011.11011)_2 = (?)_8$
- l) With circuit symbol, Boolean expression and truth table explain all logic gates.

### Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

Q3 Explain the Ge-diode characteristics under forward and reverse biased conditions. Draw the  $V \sim I$  characteristic curve. Indicate important voltage and current parameter. Compare the  $V \sim I$  curve to that of a Si diode. Mention some application of diode. (16)

Q4 Explain with a neat sketch, the structure and the working of a n-channel JFET. Draw its drain and transfer characteristic curve. Mention its application. (16)

Q5 Describe the use of operational amplifier as inverting and non-inverting amplifier. (16)

Q6  $f_1 = \_ \_ \_$   
(16)

f2 =

=

-

(i) Simplify the above functions. Draw the original and simplified circuit.

(ii) Express f1 and f2 in standard SOP form.

(iii) Express f1 and f2 in standard POS form.